

MEEC/MIEEC

RADIO FREQUENCY ELECTRONICS

Low Noise Amplifier - Part I

Authors:

Martim Duarte Agostinho (70392) Francisco Simões Coelho Sá da Costa (70386) Sofia Margarida Mafra Dias Inácio (58079)

```
md.agostinho@campus.fct.unl.pt
fsc.costa@campus.fct.unl.pt
sm.inacio@campus.fct.unl.pt
```



Contents

1	Intr	oduction	3
2	Design of the LNA		
	2.1	Transistor Bias Network	3
	2.2	S-parameters with packaging effects	3
		Transistor validation for the given bias point	
	2.4	Stability	
	2.5	Input and output matching networks	
		Gain and Noise Factor	
3	Simulation		
	3.1	Validation of the LNA design	3
		Input and output matching networks design optimization	
4	Conclusion		3

MEEC/MIEEC 1



List of Figures

MEEC/MIEEC 2

1 Introduction

2 Design of the LNA

- 2.1 Transistor Bias Network
- 2.2 S-parameters with packaging effects
- 2.3 Transistor validation for the given bias point
- 2.4 Stability
- 2.5 Input and output matching networks
- 2.6 Gain and Noise Factor
- 3 Simulation
- 3.1 Validation of the LNA design
- 3.2 Input and output matching networks design optimization
- 4 Conclusion

MEEC/MIEEC 3