

# Application Note No. 018

A Low-Noise-Amplifier at 900 MHz using SIEGET  
BFP420

Small Signal Discretes



Never stop thinking

**Edition 2006-10-27**

**Published by  
Infineon Technologies AG  
81726 München, Germany**

**© Infineon Technologies AG 2006.  
All Rights Reserved.**

## **LEGAL DISCLAIMER**

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

## **Information**

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office ([www.infineon.com](http://www.infineon.com)).

## **Warnings**

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

---

**A Low-Noise-Amplifier at 900 MHz using SIEGET BFP420****Revision History: 2006-10-27, Rev. 2.0****Previous Version: 2000-07-27**

| Page | Subjects (major changes since last revision) |
|------|--|
| All  | Document layout change                       |
|      |  |
|      |  |
|      |  |
|      |  |
|      |  |
|      |  |
|      |  |
|      |  |
|      |  |

**Trademarks**

SIEGET® is a registered trademark of Infineon Technologies AG.


## A Low-Noise-Amplifier at 900 MHz using SIEGET BFP420

### 1 A Low-Noise-Amplifier at 900 MHz using SIEGET BFP420

This application note describes a low noise amplifier at 900 MHz using SIEMENS SIEGET®25 BFP420. The design emphasis has been on achieving low noise figure. A circuit description, schematic, PCB layout and components list are shown below together with measured performance data.

#### Data at 0.9 GHz (3 V and 5 mA)

|                 |         |
|-----------------|---------|
| Gain:           | 18 dB   |
| $IP_{3out}$ :   | 10 dBm  |
| NF:             | 1.35 dB |
| $R_{Lin-out}$ : | >10 dB  |

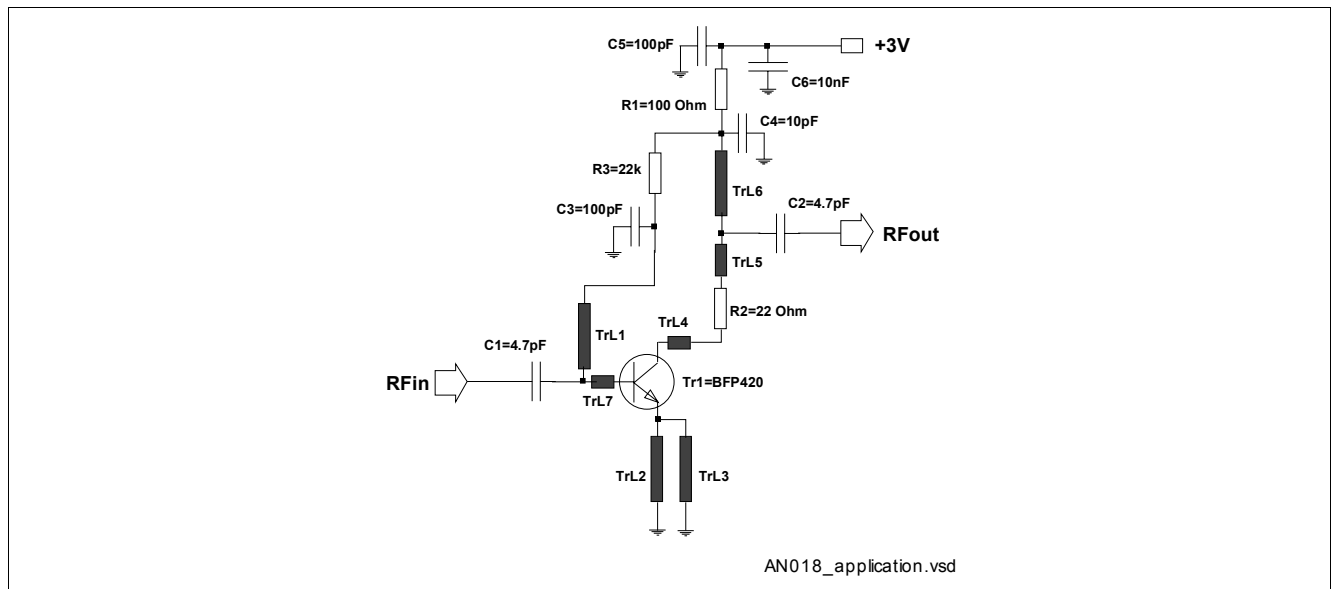


**Figure 1 Application**

This amplifier at 900 MHz has been realized by using microstrip lines as matching elements. The design offers a good compromise between high  $IIP_3$ - values, low noise figure and high return loss.

In order to optimize the design for a particular application please observe the following points:

- The layout size can be reduced by using chip inductors instead of the microstrip lines TrL1 and TrL6
- Improved stabilization behaviour versus temperature and reduced variation in amplifier performance due to the device's Beta (current gain) distribution can be achieved by using an active bias circuit. Such a circuit is available as a single device from Infineon - BCR400. For further information please refer to Application Note No.14. However, the resistors R1 and R3 are sufficient in most applications for stabilization purposes.
- This circuit is not optimized, for low noise figure, it is a first step to a good design. The measured figures include losses of SMA-connectors and the relatively high loss of the microstrip lines on the epoxy-board.
- The use of teflon material would provide an improvement of  $\approx 0.1$  dB.
- Resistor R2 is used to get higher RF-circuit-stability and return loss values at the output. It also affects the output intermodulation performance.

## A Low-Noise-Amplifier at 900 MHz using SIEGET BFP420

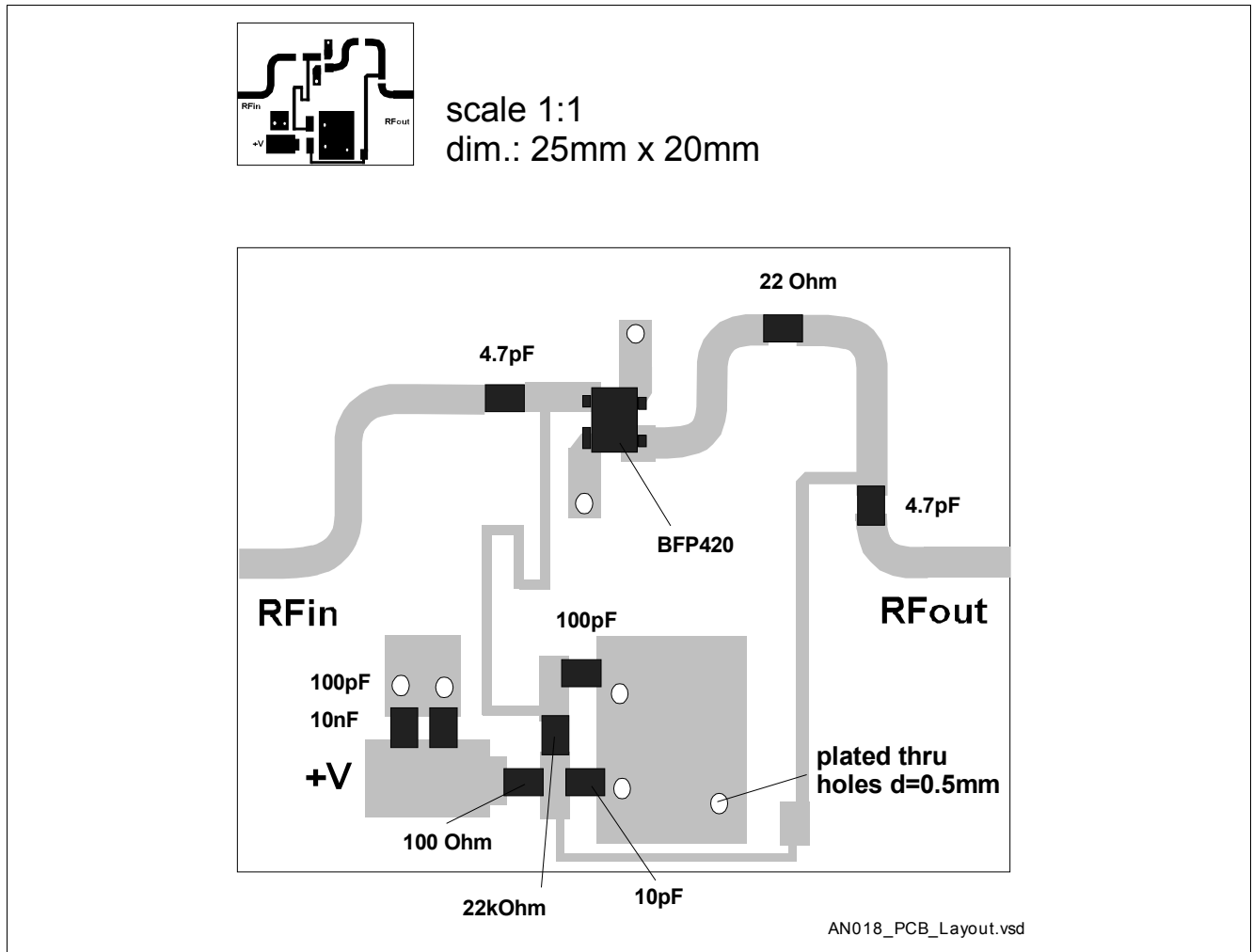

**Figure 2** PCB Layout and Component Placement


# A Low-Noise-Amplifier at 900 MHz using SIEGET BFP420

**Table 1 Component**

| Component | Value | Unit      | Size   | Comment  |
|-----------|-------|-----------|--------|--|
| R1        | 100   | $\Omega$  | 0603   | Bias / collector-resistance / $V_{R1} \cong 0.5 \text{ V}$ |
| R2        | 22    | $\Omega$  | 0603   | To improve stability and output return loss                |
| R3        | 22    | $k\Omega$ | 0603   | Bias / base-resistor                                       |
| C1        | 4.7   | pF        | 0603   | Input match  |
| C2        | 4.7   | pF        | 0603   | Output match   |
| C3        | 100   | pF        | 0603   | RF-short   |
| C4        | 10    | pF        | 0603   | Output match   |
| C5        | 100   | pF        | 0603   | RF-short   |
| C6        | 10    | nF        | 0603   | RF-short   |
| Tr1       |       |           | SOT343 | SIEGET® BFP420   |
| TrL1      |       |           |        | Input match and bias, w = 0.3 mm                           |
| TrL2      |       |           |        | Emitter-microstrip-line, w = 0.95 mm                       |
| TrL3      |       |           |        | Emitter-microstrip-line, w = 0.95 mm                       |
| TrL4      |       |           |        | Output match, w = 0.95 mm                                  |
| TrL5      |       |           |        | Output match, w = 0.95 mm                                  |
| TrL6      |       |           |        | Output match and DC-bias, w = 0.95 mm                      |
| TrL7      |       |           |        | Input match, w = 0.95 mm                                   |
| Substrate | FR4   |           |        | $h = 0.5 \text{ mm}$ , $\epsilon_r = 4.5$                  |

# A Low-Noise-Amplifier at 900 MHz using SIEGET BFP420

## Measurements

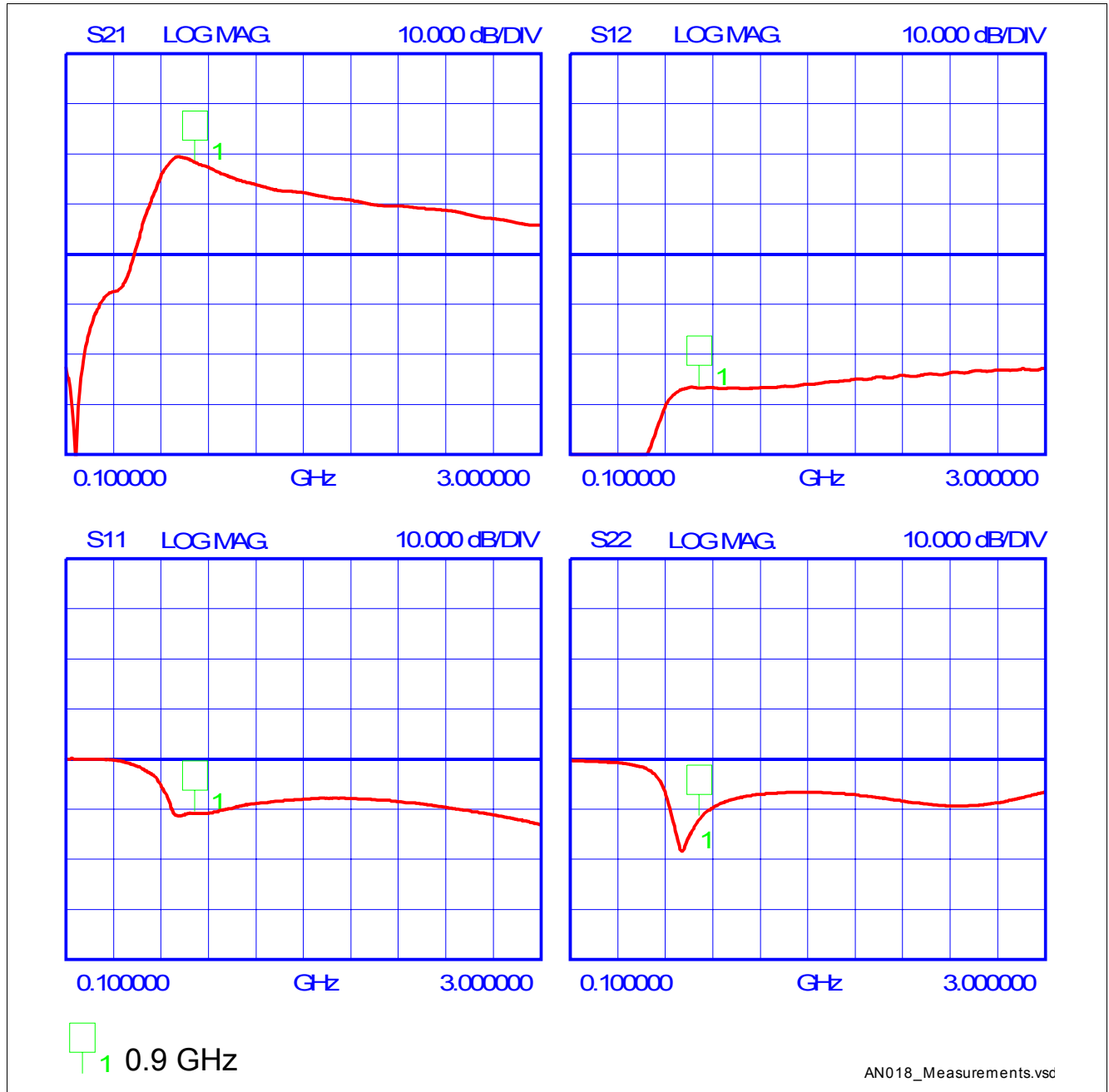

**Figure 3** Measurements